


① Assuming,
Initially Both switches (S_1, S_2) are "off" & Light is "off"
(L)

	Switch(S_1)	Switch(S_2)	Light (L)
Initial \rightarrow	0	0	0
\Rightarrow	1	0	1
	1	1	0
	0	1	1

$$S_1 \bar{S}_2 + S_2 \bar{S}_1 = L$$

$$(or) L = S_1 \oplus S_2$$

Logical Circuit

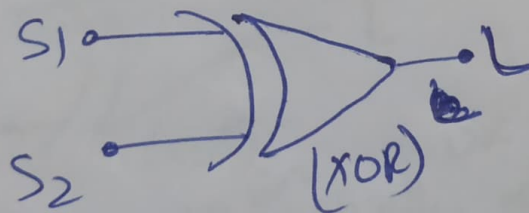

In our homes, for a two way switch we can either use "AOI" (or) "XOR" logic. so possibly "yes."

(Method 1)

② We know that

①

Assumptions

* $C_1, C_0 \neq 0, 0$

* If $C_1, C_0 = 0, 1$ Remainder $R_1, R_0 = 0, 0$

* If $D_2 = 0$ & $C_1, C_0 = D_1, D_0$ Remainder $R_1, R_0 = 0, 0$

* $D_2 D_1 D_0 > C_1 C_0$

So remaining cases possible are.

(Remainder %)	$D_2 D_1 D_0$	$C_1 C_0$	$R_1 R_0$
3%2	0 1 1	1 0	0 1
4%2	1 0 0	1 0	0 0
4%3	1 0 0	1 1	0 1
5%2	1 0 1	1 0	0 1
5%3	1 0 1	1 1	1 0
6%2	1 1 0	1 0	0 0
6%3	1 1 0	1 1	0 0
7%2	1 1 1	1 0	0 1
7%3	1 1 1	1 1	0 1

Note $(D_2 D_1 D_0)_{\max} = 7 \Rightarrow 111$
 $(C_1 C_0)_{\max} = 3 \Rightarrow 11$

If $D_2 D_1 D_0 < C_1 C_0$
 Remainder is always
 " $C_1 C_0$ "
 i.e. " $R_1 R_0$ " = " $C_1 C_0$ "

We can include (iii) next to
 for our convenience.

To Include this,
 we can simply follow
 the method ②

"Kmaps" is not must
 as sir mentioned.

(Include)

Two outputs

R_1, R_0

For R_1

$D_2 D_1 D_0$	$C_1 C_0$	R_1
1 0 1	1 1	1

$R_1 = D_2 \bar{D}_1 D_0 C_1 C_0$

⑥

For R_0

$D_2 D_1 D_0$	$C_1 C_0$	R_0
0 1 1	1 0	1
1 0 0	1 1	1
1 0 1	1 0	1
1 1 1	1 0	1
1 1 1	1 1	1

$R_0 = \bar{D}_2 D_1 D_0 C_1 \bar{C}_0$
 $+ D_2 \bar{D}_1 \bar{D}_0 C_1 C_0$
 $+ D_2 \bar{D}_1 D_0 C_1 \bar{C}_0$
 $+ D_2 D_1 D_0 C_1 \bar{C}_0$
 $+ D_2 D_1 D_0 C_1 C_0$

Method 2

②

Simply assume $C_1, C_0 \neq 0$ among

$\odot 01, 10, 11$

"Brute force"
②

D_2	D_1	D_0	C_1	C_0	R_1	R_0
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	0	1	1	0	0
0	0	0	0	1	0	1
0	0	1	1	0	0	1
0	0	1	1	1	0	0
0	0	1	0	1	0	0
0	1	0	1	0	1	0
0	1	0	1	1	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	0	1	1	0	0
0	1	1	0	1	0	1
0	1	1	1	0	0	0
0	1	1	1	1	0	0
1	0	0	0	1	0	1
1	0	0	1	0	1	0
1	0	0	1	1	1	0
1	0	1	0	1	0	0
1	0	1	1	0	1	0
1	0	1	1	1	1	0
1	1	0	0	1	0	0
1	1	0	1	0	1	0
1	1	0	1	1	1	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0
1	1	1	1	1	1	0

③



$$R_1 = \bar{D}_2 D_1 \bar{D}_0 C_1 C_0 + D_2 \bar{D}_1 D_0 C_0 C_1$$

$$R_0 = \bar{D}_2 \bar{D}_1 D_0 C_1 \bar{C}_0 + \bar{D}_2 \bar{D}_1 D_0 C_1 C_0 + \bar{D}_2 D_1 D_0 C_1 \bar{C}_0 + D_2 \bar{D}_1 \bar{D}_0 C_1 C_0 + D_2 \bar{D}_1 D_0 C_1 \bar{C}_0 + D_2 D_1 \bar{D}_0 C_1 C_0 + D_2 D_1 D_0 C_1 \bar{C}_0$$

20

Method 1



Circuit Schematic

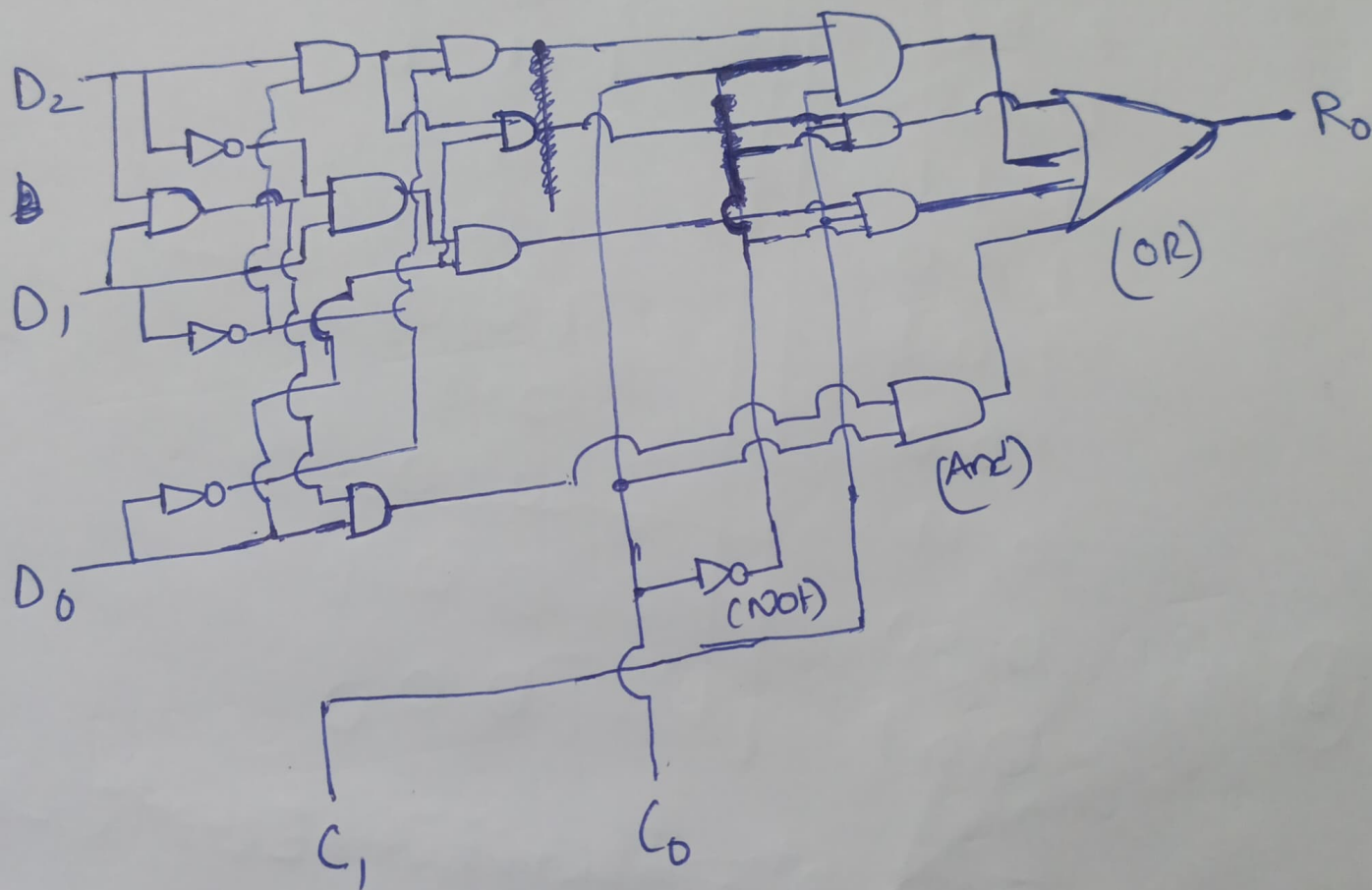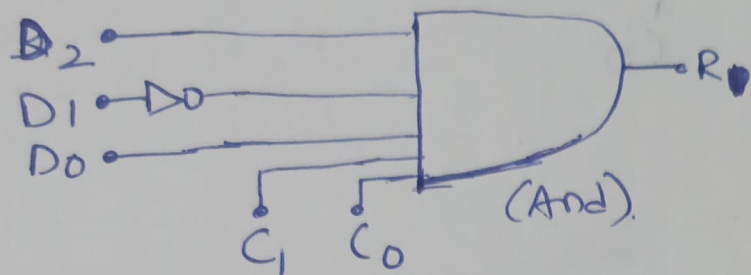


Similarly for method 2

③ States

(a)

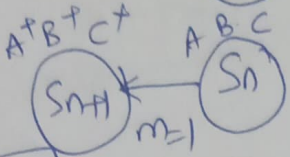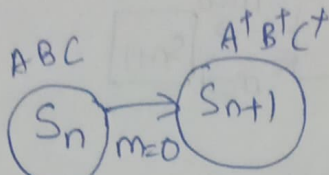

In a simpler way

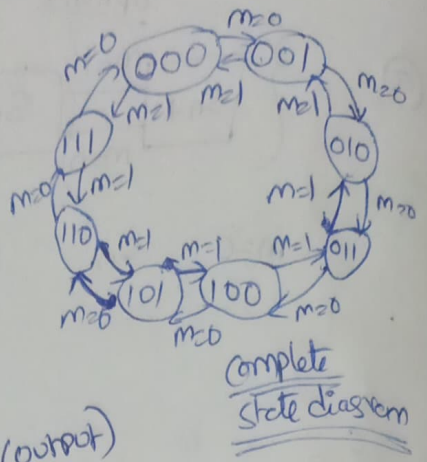

complete state diagram

Truth table

$m=0$ S_n (Input)

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

S_{n+1} (output)

A^+	B^+	C^+
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

$m=1$

S_n (Input)

A	B	C
0	0	0
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1

S_{n+1} (output)

A^+	B^+	C^+
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

(b)

For $m=0 \Rightarrow \bar{m}$

$$A^+ = \bar{A}BC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} = \bar{A}\bar{B} + B(\bar{A}\bar{C})$$

$$B^+ = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B\bar{C} = \bar{B}\bar{C} + \bar{B}C$$

$$C^+ = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}C + \bar{A}B\bar{C} = \bar{A}\bar{C} + \bar{A}C = \bar{C}$$

for $m=1$

$$A^+ = \bar{A}\bar{B}\bar{C} + AB\bar{C} + AB\bar{C} + AC\bar{B} = AB + \bar{B}$$


$$B^+ = \bar{A}\bar{B}\bar{C} + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} = \bar{B}\bar{C} + BC$$

$$C^+ = \bar{A}\bar{B}\bar{C} + AB\bar{C} + \bar{A}B\bar{C} + AB\bar{C} = \bar{C}$$


$$\Rightarrow A^+ = \bar{m}(AB + B(A \oplus C)) + m(AB + \bar{B})$$

$$B^+ = \bar{m}(\bar{B}\bar{C} + \bar{B}C) + m(\bar{B}\bar{C} + BC)$$
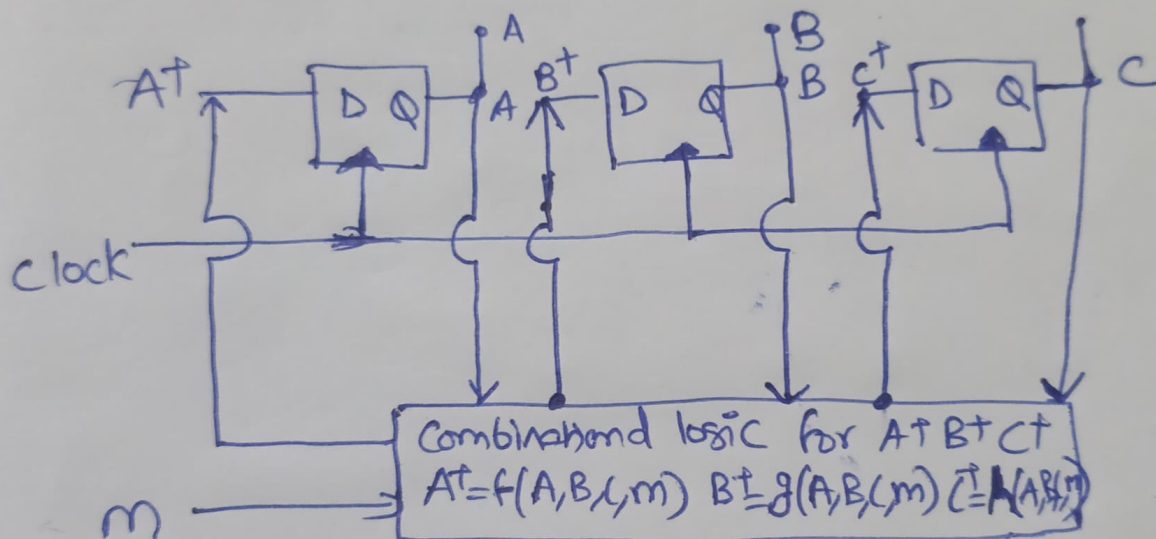
$$C^+ = \bar{m}(\bar{C}) + m(\bar{C}) = \bar{C}$$



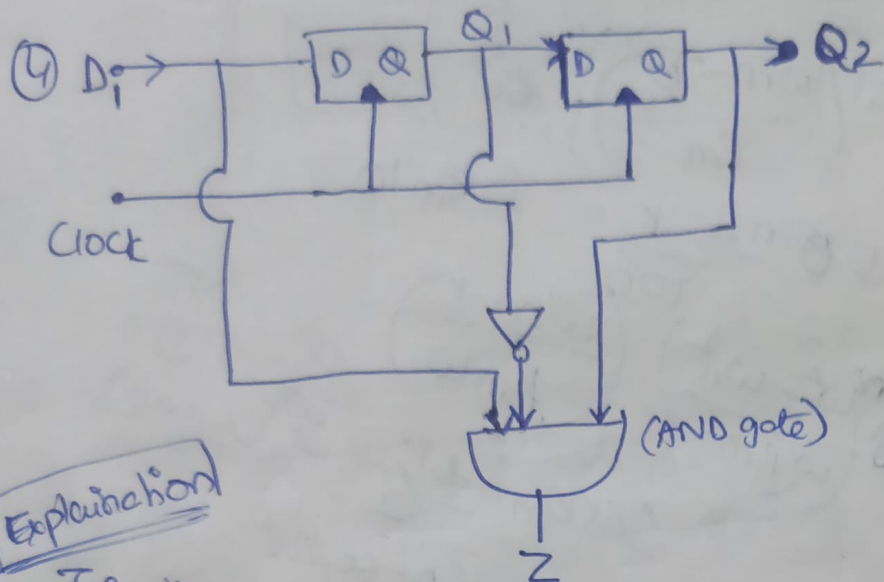A^+, B^+, C^+ are evaluated using combinational logic from current values of A, B, C & " m "



Explanation

Initially (Let's assume sequence to be exactly as "101") (ie $D_1 \rightarrow 1 \rightarrow 0 \rightarrow 1$)

" " D_1 is the Input Given continuously for every clock cycle

Clock	<u>D_1</u>	<u>Q_1</u>	<u>Q_2</u>	<u>Z</u>
1	1	0	0	0
0	0	1	0	0
1	1	0	1	1

$$Z = D_1 Q_1 Q_2$$

In order to get our output high, we need to use current value of " D_1 " & remember earlier "2" values of " D_1 ", So two flipflops are needed to remember.