

ME 311: Microprocessors and Automatic Control

Microprocessor interfacing PWM interface



P.S. Gandhi
Mechanical Engineering
IIT Bombay

PRASANNA S GANDHI
gandhi@me.iitb.ac.in

1



Various interfaces

- Digital input output (I/O)
- PWM: Pulse width modulation
- Counter interface
- Analog to digital converter ADC
- Digital to analog converter DAC
- Communication interfaces: uart, RS232, etc.

PRASANNA S GANDHI gandhi@me.iitb.ac.in

2



Philosophy of Interfacing

- Although we saw specific digital i/o interfaces in detail with example of 8085 microprocessor and XEP 100, what you need to take away is philosophy rather than syntax
- Basic philosophy in all interfacing problems is to write specific 'words' in different registers. Control word in control register and so on.
- The syntax of these words is what is to look for in the data sheet of the respective micro-controller
- Say for example look at data sheet of XEP 100 to program the PWM interface.

PRASANNA S GANDHI gandhi@me.iitb.ac.in

3



Philosophy of Interfacing: PWM

- Q: What is PWM?
- Q: Why we need PWM interface in automatic control application?
- Problem statement: Given PWM frequency say 10 Khz and duty cycle say x % develop a program to initiate different registers in XEP 100 to achieve corresponding PWM output on channel 1.

PRASANNA S GANDHI gandhi@me.iitb.ac.in

4



What all we need to run motor using muc?


- Q: does microcontroller have large power needed to drive motors? NO 😞
- So some kind of **power amplifier** is needed
- What would be input to this power amplifier?
- How to regulate power/voltage given to motor and how to change the direction? Any ideas!!!

PRASANNA S GANDHI gandhi@me.iitb.ac.in

5



Power Amplifier

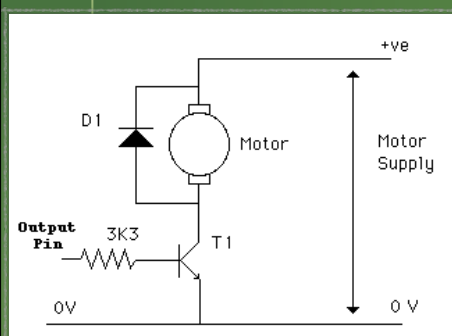


- Lets look at simple power amplifier circuit we know: power transistor
- Would this work
 - How do we vary power
 - How do we change direction?

PRASANNA S GANDHI gandhi@me.iitb.ac.in

6



Power Amplifier

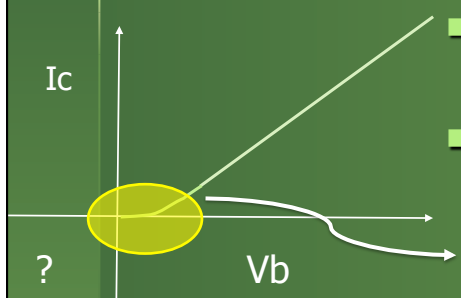

- Reverse characteristics not favorable to change direction of motor

- Recall transistor characteristics

- Problems

- Forward bias voltage is required before current can flow

- Which input from microprocessor can vary power?


- Analog / Digital??

PRASANNA S GANDHI gandhi@me.iitb.ac.in

7



How do we get over these problems?

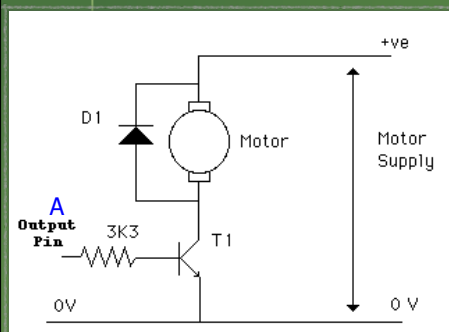

- Can we use digital input instead of analog input at **A** in smart way to deliver varying power?

- How to vary power?

- Switch on and off digital signal at **A**. Vary 'on time' as compared to 'off time'


PRASANNA S GANDHI gandhi@me.iitb.ac.in

8



What do we achieve?

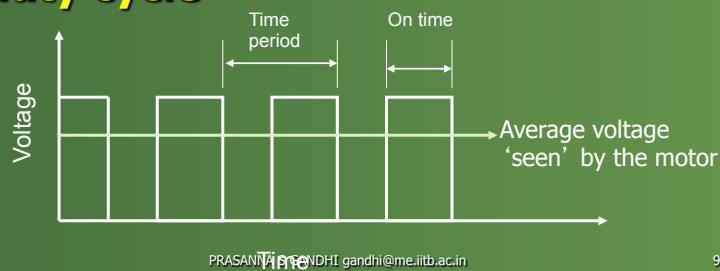- Pulse Width Modulation (PWM): Power supply regulated by varying the % of “on-time” of a digital signal also called **duty cycle**




9



What do we achieve?

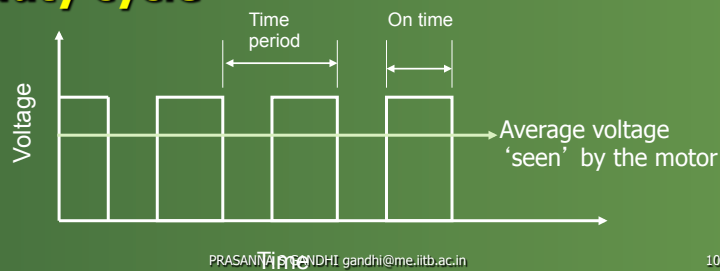
- Pulse Width Modulation (PWM): Power supply regulated by varying the % of “on-time” of a digital signal also called **duty cycle**



10



What do we achieve?

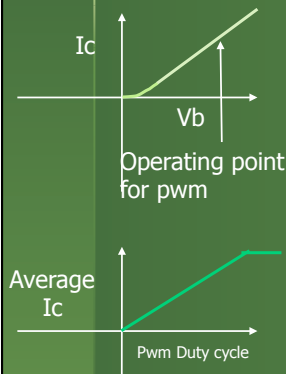

- Operating point on transistor characteristics is now fixed. Issue related to “dead zone” disappear.
- Smooth variation of average I_c in motor by varying “on time” of PWM waveform.
- **IMP: PWM frequency should be high 'enough' : typically 2-10 kHz**

PRASANNA S GANDHI gandhi@me.iitb.ac.in

11




PWM interface of XEP 100

- Identify registers and their values to be used from datasheet of XEP 100
- Specifically look at PWME, PWMCLK, PWMPOL, PWMPRCLK, PWMDTYx, PWMPERx registers in datasheet
- Use PWMPERx = 0xFF value. Think why??
- C program for generating desired PWM signal on channel 1 will finally be like setting some values into these registers

PRASANNA S GANDHI gandhi@me.iitb.ac.in

12

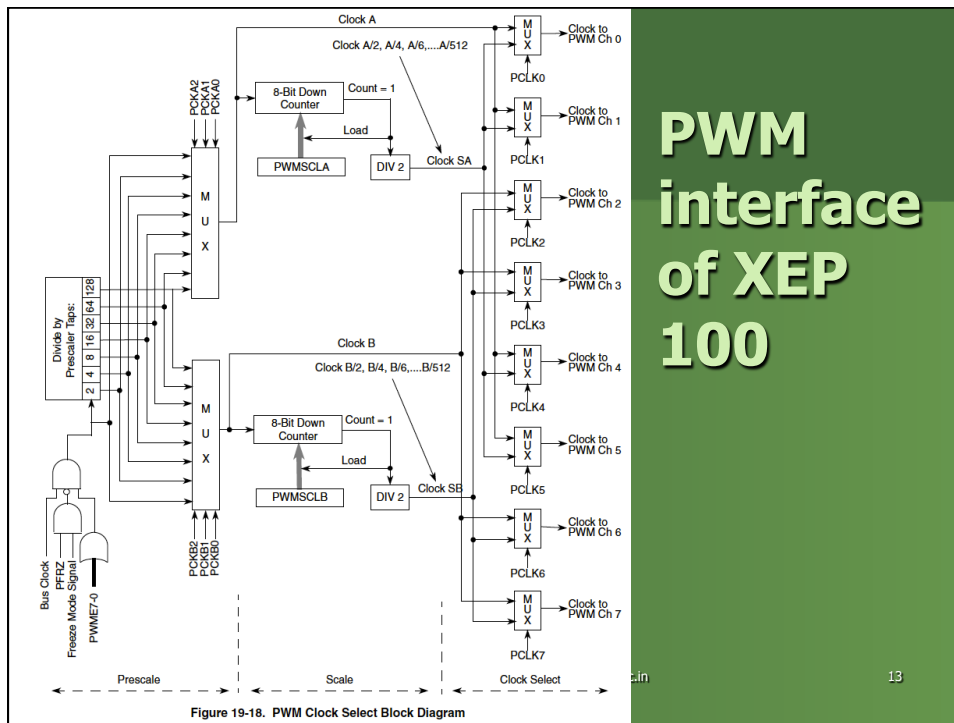

Reminder: what is mux!!

Multiplexer

I0	I1	A	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


Simplest:

- Two data inputs I0 and I1 and control input A
- Depending on A select either I0 or I1

$$Z = A' I_0 + A I_1$$

A	Z
0	I0
1	I1

PRASANNA S GANDHI gandhi@me.iitb.ac.in

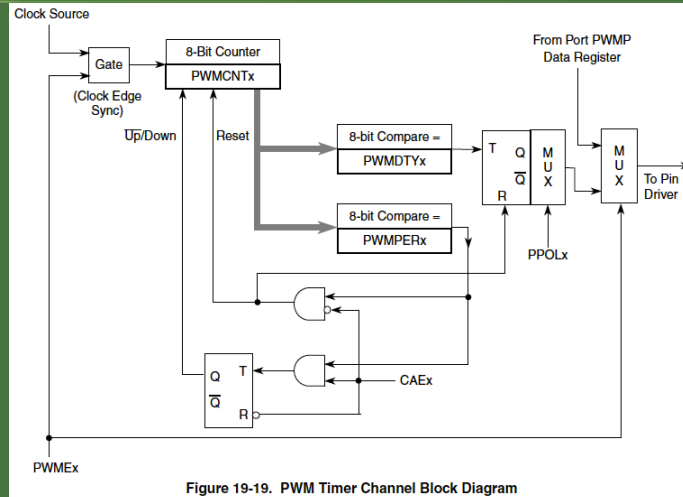

15



- See datasheets



DAC: Digital to analog converter

- Given digital number how to generate voltage corresponding to the value?
- Electronic circuit to do so? Can you think of a circuit
- Use opamps to achieve this

PRASANNA S GANDHI gandhi@me.iitb.ac.in


17



Using Opamp for summing

Summing amplifier with Binary weighted Input Resistors

$$\begin{aligned} V_o &= -R_f I_T \\ &= -(1k)(0.875 \text{ mA}) \\ &= -0.875 \text{ V} \\ &= |7/8 \text{ V}| \end{aligned}$$

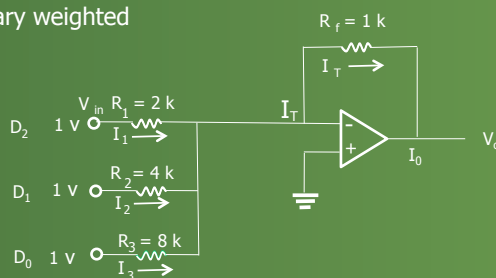


PRASANNA S GANDHI gandhi@me.iitb.ac.in

18



A 3-Bit A/D Converter

Quantization problem!!

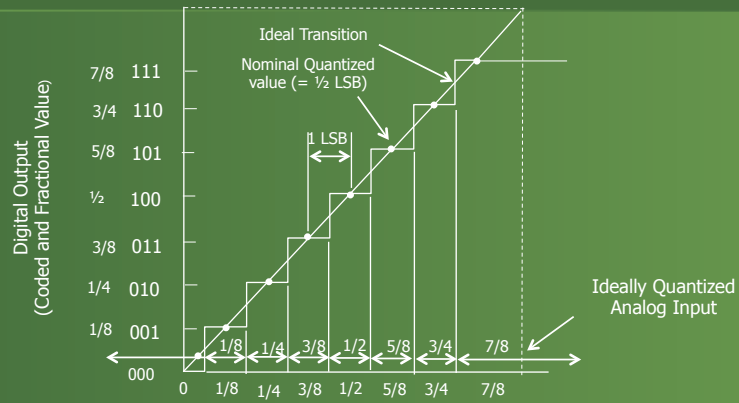

(b) Analog Input vs Digital Output

PRASANNA S GANDHI gandhi@me.iitb.ac.in

19



Thank You

PRASANNA S GANDHI gandhi@me.iitb.ac.in

20